
AIUB COURSE SOLUTION

ELECTRICAL CIRCUITS-02 (AC)
SPRING 16-17

MANNAN SIR'S MID-TERM ASSIGNMENT
NUMBER-02 SOLUTION





TOGETHER WE CAN ACHIEVES MORE

American International University-Bangladesh (AIUB)
Engineering Faculty
EEE 2101: Electrical Circuits-2 (AC)





Assignment 02 [Total 10 Marks]

Submission Date	Marks	Tick on following
With in March 09, 2017	10	
March, 12, 2017 to March 13, 2017	8	
March, 14, 2017 to March 15, 2017	4	
After Feb. 23, 2017	0	

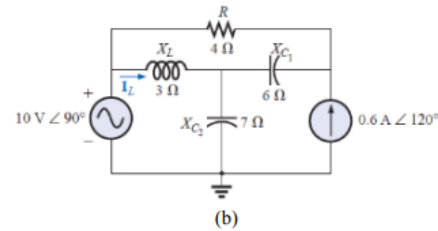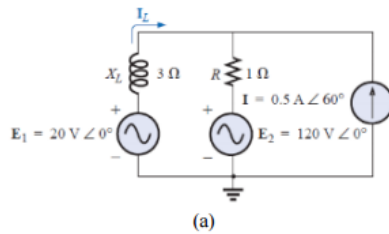[1] Using superposition, determine the current through the inductance X_L for each network as shown in the following figure.




- [2] (i) Find the Thévenin equivalent circuit (Z_{TH} and E_{TH}) at the terminal of load impedance Z_L . Draw the Thevenin equivalent circuit.
(ii) Find the Norton equivalent circuit (Z_N and E_N) at the terminal of load impedance Z_L . Draw the Thevenin equivalent circuit.
(iii) Find the value of load impedance to received maximum power.
(iv) Calculate the maximum power consumed by load impedance.

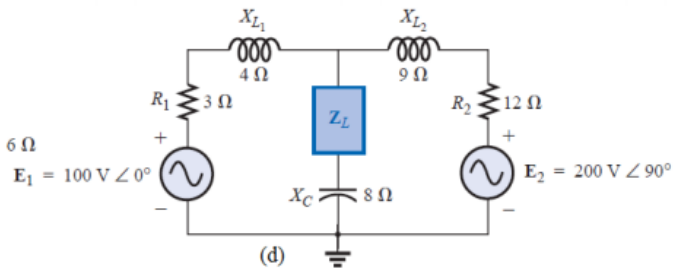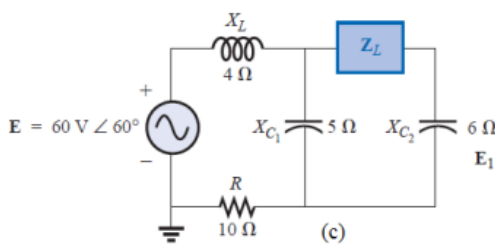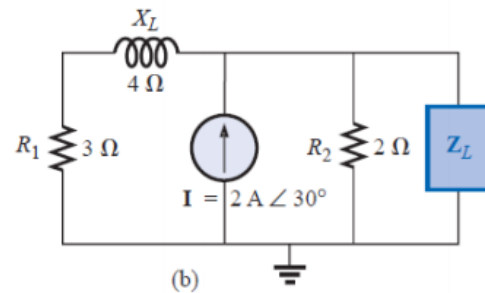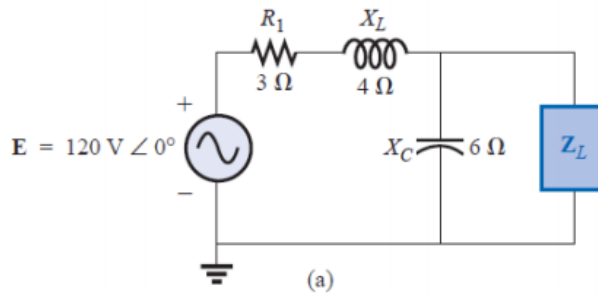


Answer of 1:


(a)

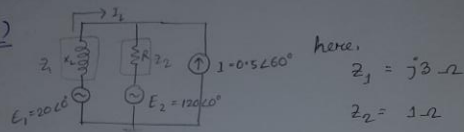

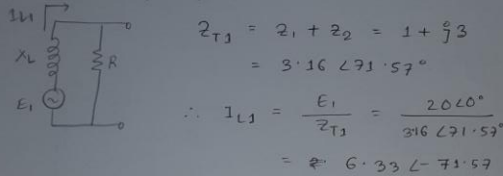
i) consider $E_1 = 20\angle 0^\circ$, $E_2 = 0$ (short) and $I = 0$ (open)



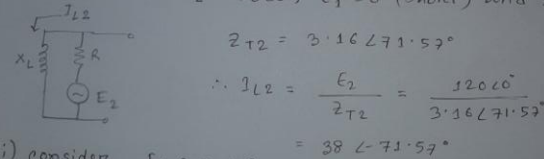ii) consider $E_2 = 120\angle 0^\circ$, $E_1 = 0$ (short) and $I = 0$ (open)



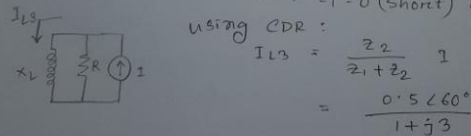(iii) consider $I = 0.5\angle 60^\circ$, $E_1 = 0$ (short) and $E_2 = 0$ (short)



$$\therefore I_{L3} = 0.16 \angle -11.57^\circ$$


$$\therefore \text{Total } I_L = I_{L1} - I_{L2} - I_{L3}$$

$$= (6.33 \angle -71.57^\circ) - (38 \angle -71.57^\circ) - (0.16 \angle -11.57^\circ)$$

$$= 31.77 \angle 108.73^\circ \quad (\text{Ans})$$


Q Answer of 2:

(a)

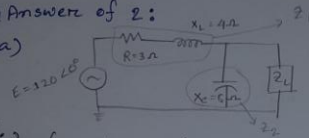

here,
 $z_1 = 3 + 4j$
 $z_2 = -6j$


(i) for thevenin's:

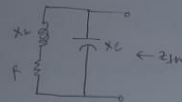

$$Z_{th} = z_1 \parallel z_2$$

$$= \frac{(3 + 4j)(-6j)}{3 + 4j - 6j}$$

$$= 8.31 - j0.46$$

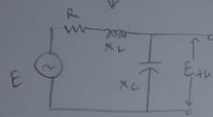


using VDR:

$$E_{th} = \frac{z_2}{z_1 + z_2} \times E$$

$$= \frac{-6j}{3 + 4j - 6j} \times (120 \angle 0^\circ)$$

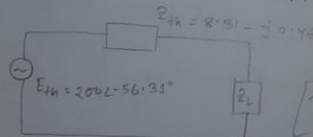
$$\therefore E_{th} = 200 \angle -56.31^\circ$$



[Thevenin's Equivalent Circuit]


(ii) for Norton's :-

$$Z_N = Z_{th} = 8.31 - j0.46$$

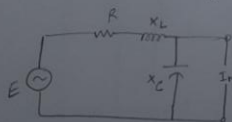

$$I_N = \frac{E}{z_1} = \frac{120 \angle 0^\circ}{3 + j4}$$

$$= 24 \angle -53.13^\circ$$

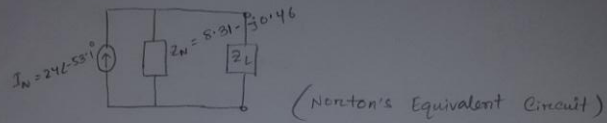


(iii) Value of Load Impedance:

$$Z_{\text{load}} = Z_{\text{th}}^* = 8.31 - j0.46$$


(iv) The maximum power:

$$P_{\text{max}} = \frac{E_{\text{th}}^2 (\text{rms})}{4 \times R_{\text{load}}} = \frac{(200)^2}{4 \times 8.32}$$

$$= 1201.92 \text{ W (Ans.)}$$

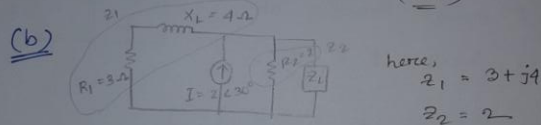

(i) for thevenin's:

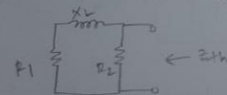


here, $I = 0$ (open)

$$Z_{\text{th}} = Z_1 \parallel Z_2$$

$$= \frac{(3 + j4)(2)}{3 + j4 + 2}$$

$$= 1.5 + j0.4$$

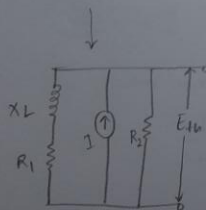


Using CDR:

$$I_{R2} = \frac{Z_2 Z_1}{Z_1 + Z_2} \times I$$

$$= \frac{3 + j4}{3 + j4 + 2} (2 \angle 30^\circ)$$


$$= 0.31 - j0.05$$
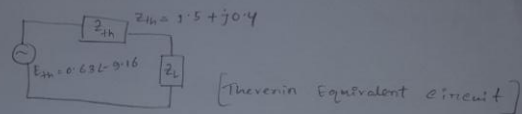
$$\begin{aligned} \therefore E_{th} &= I_2 \times Z_2 \\ &= (0.31 - j0.05) \times 2 \\ &= 0.62 \angle -9.16^\circ \end{aligned}$$




(ii) for Norton's :

$$Z_N = 1.5 + j0.4$$

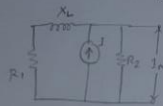

here, Z_1 and Z_2 is parallel to current source 'I' :
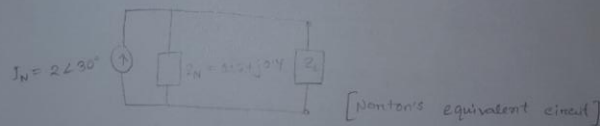
$$\therefore I_N = I = 2 \angle 30^\circ$$




(iii) Value of load Impedance :

$$Z_{load} = Z_{th}^* = 1.5 - j0.4$$

(iv) The maximum power :

$$P_{max} = \frac{E_{th}^2}{4 \times R_{load}} = \frac{(0.62)^2}{4 \times 1.5} = 0.1 \text{ W}$$


(c)

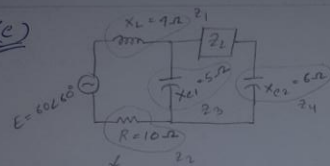

here,

$$\begin{aligned} Z_1 &= j4 \\ Z_2 &= 10 \\ Z_3 &= -5j \\ Z_4 &= -6j \end{aligned}$$

(i)

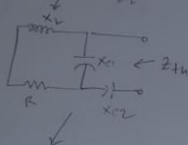


$$\begin{aligned} Z_{th} &= \frac{(Z_1 + Z_2) Z_3}{Z_1 + Z_2 + Z_3} + Z_4 \\ &= \frac{(10 + 4j)(-5j)}{10 + 4j - 5j} + (-6j) \end{aligned}$$

$$\therefore Z_{th} = 2.5 - 4.8j$$

using NDR:

$$\begin{aligned} E_{th} &= \frac{Z_3}{(Z_1 + Z_2) + Z_3} \times E \\ &= \frac{-6j}{10 + 4j - 6j} (60 \angle 60^\circ) \end{aligned}$$

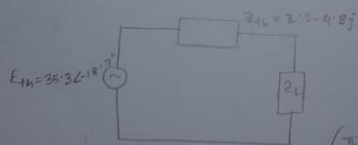
$$\therefore E_{th} = 35.3 \angle -18.7^\circ$$



(Thevenin's Equivalent Circuit)

(ii) for Norton's:

$$Z_N = Z_{th} = 2.5 - j4.8$$

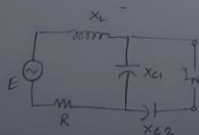


here,

$$\begin{aligned} Z_1 &= 10 + 4j + \frac{(-5j)(-6j)}{(-5j - 6j)} \\ &= 10 + 1.8j \end{aligned}$$

$$I_T = \frac{E}{Z_T} = \frac{60 \angle 60^\circ}{10 + j1.3} = 3.6 + j4.73j$$

$$\therefore I_N = \frac{(-5j)}{-5j - 6j} (3.6 + j4.73j) \quad [\text{using CDR}]$$
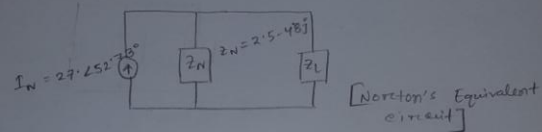
$$\Rightarrow I_N = 1.64 + j2.15 = 2.7 \angle 52.73^\circ$$





(iii) Value of load impedance:

$$Z_{\text{load}} = Z_{th}^* = 2.5 + j4.8$$

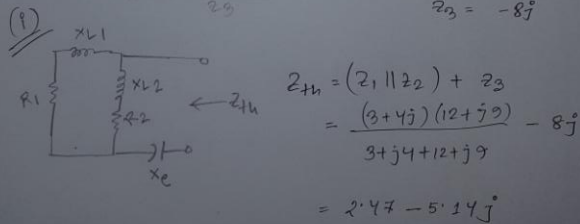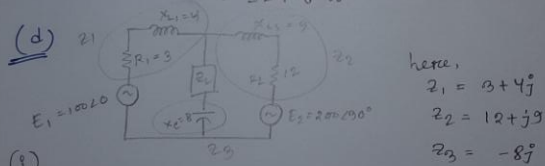(iv) The maximum power:

$$P_{\text{max}} = \frac{E_{th}^2(\text{rms})}{4 \times R_{\text{load}}} = \frac{(35.3)^2}{4 \times 2.5} = 124.6 \text{ W}$$



for E_{th} :-

considering $E_1 = 0$




$$E_{th1} = \frac{Z_1}{Z_1 + Z_2} \times E_2$$

$$= \frac{3 + j4}{3 + j4 + 12 + j9} (200 \angle 96^\circ)$$

$$\therefore E_{th1} = 50.4 \angle 102.22^\circ$$

considering $E_2 = 0$;

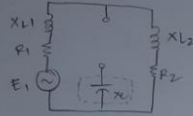


$$E_{th2} = \frac{Z_2}{Z_1 + Z_2} \times E_1$$

$$= \frac{12 + j9}{3 + j4 + 12 + j9} (100 \angle 0^\circ)$$

$$\therefore E_{th2} = 75 \angle -4.04^\circ$$

$$\therefore E_{th} = E_{th1} + E_{th2} = (50.4 \angle 102.22^\circ + 75 \angle -4.04^\circ)$$

$$= 77.77 \angle 94.49^\circ$$

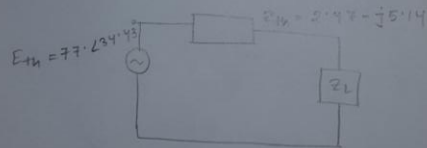

(ii) for Norton's :-

$$Z_N = Z_{th} = 2.47 - j5.14$$

for I_N :-

considering $E_1 = 0$;



$$R_T = \frac{z_1 z_2}{z_1 + z_2} + z_2$$

$$= \frac{(3+4j)(-8j)}{3+4j-8j} + (12+9j)$$


$$= 19.7 + j11.24$$

$$I_T = \frac{E_2}{R_T} = \frac{200 \angle 90^\circ}{19.7 + j11.24} = 4.38 + j7.77$$

$$\therefore I_{N1} = \frac{4+8j}{3+4j-8j} (4.38 + j7.77)$$

$$= 8.86 \angle 166.63^\circ$$

considering $E_2 = 0$;

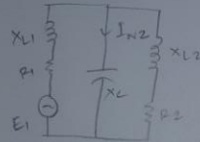

hence,

$$Z_T = \frac{z_2 z_2}{z_2 + z_2} + z_1$$

$$= \frac{(12+j9)(-8j)}{12+j9-8j} + 3+4j$$

$$= 8.3 - 4.44j$$


$$I_T = \frac{E_1}{Z_T} = \frac{100 \angle 0^\circ}{8.3 - 4.44j} = 9.37 + 5.02j$$

$$I_{N2} = \frac{12+j9}{12+j9-8j} (9.37 + 5.02j)$$

$$= 13.24 \angle 60.28^\circ$$

$$\therefore I_N = I_{N1} + I_{N2} = 8.86 \angle 166.63^\circ + 13.24 \angle 60.28^\circ$$

$$= 13.7 \angle 98.63^\circ$$

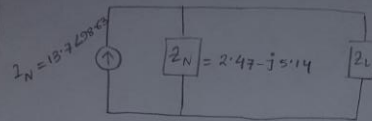

(Norton's Equivalent circuit)

(iii) value of load impedance:

$$Z_{load} = Z_N^* = 2.47 + j5.14$$

(iv) maximum power:

$$P_{max} = \frac{E_{th(rms)}^2}{4 \times R_{load}} = \frac{(77.77)^2}{4 \times 2.47}$$

$$= 612.16 \text{ W (Ans.)}$$